Tabela wzbolzen przerzutnika JK:

9	q _o	jk
0	0	οx
0	1	1 ×
1	0	× 1
1	1	X D

Tworzymy pomocnicza tobeleldz wantościami joko jaka:

Na poolstowie pomocniczej tobeli (1)

tworzymy tobele stanow (2) golzie: qo,q, to
alstaalne stany przerzutników JK;

x, y - wej saioi

que, q, - nowe stany przerzutników

z - wyjsnie zowtomota

40 Va	×Υ	900 dos	2	
00	00	10	0	
00	01	00	0	
00	10	11	0	
00	11	0.1	0	
01	00	00	1	
01	01	00	0	
01	10	11	0	
01	11	11	6	
10	00	10	1	
-10	0 1	10	0	
10	10	00	0	
10	11	10	0	
11	06	10	1	
11	01	10	0	
11	10	10	0	
11	11	10	0	
- (-)	, ,	1 0	Ü	